

# EE 236: Experiment No. 6

## Study of NMOS and CMOS Characteristics

Vinamra Baghel, 190010070

March 16, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

The following were the aims of the experiment:

- To measure transfer characteristics of NMOS transistor.
- To analyse the effect of body bias on the characteristics of a NMOS transistor.
- To obtain voltage transfer characteristics of CMOS inverter.
- To obtain transfer characteristics of CMOS inverter.

### 1.2 Methods

The method overview includes constructing circuit netlists according to the standard circuit, simulating them using *dc* or *tran* analysis and calculating required parameters for all parts. The first plot required us to plot  $I_D - V_{DS}$  characteristics, and calculate  $r_{DS}$ , Early Voltage ( $V_0$ ), and  $r_0$ . The second and third plots required us to plot  $I_D - V_{GS}$  characteristics, and find  $V_T$ ,  $g_m$  and  $k$ . The further parts required us to simulate DC and Transient characteristics of a CMOS Inverter and calculate associated values such as Switching Threshold Voltage, rise time, fall time, and propagation delay.

## 2 Design

### 2.1 Part 1

The netlist according to the following circuit diagram was made which included an NMOS transistor and voltage sources.

 


Figure 1: The I-V Characterization Circuit

DC analysis was performed by varying  $V_{DS}$  from 0V to 5V in steps of 0.001V and  $V_{GS}$  from 2.5V to 4V in steps of 0.5V to obtain the I-V characteristic plots.  $R_{DS}$  in the linear region was found using:

$$R_{DS} = \frac{\Delta V_{DS}}{\Delta I_{DS}}$$

$V_0$  was found as the x-intercept of the equation in the saturation region:

$$y = mx + c$$

$R_0$  in the saturation region was found using:

$$R_0 = \frac{\Delta V_{DS}}{\Delta I_{DS}}$$

## 2.2 Part 2

$I_D$  was plotted against  $V_{GS}$ , first keeping  $V_{DS} = 200\text{mV}$  (linear) and then  $V_{DS} = 5\text{V}$  (saturation).  $V_T$  and  $g_m$  were found from the plot.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Then,  $k$  was found from the slope of the  $\sqrt{I_D}$  vs  $V_{GS}$ .

$$k = 2 \cdot \left( \frac{\Delta \sqrt{I_D}}{\Delta V_{GS}} \right)^2$$

## 2.3 Part 3

$V_{DS}$  was set to 200mV. DC analysis was performed by varying  $V_{GS}$  from 0V to 5V in steps of 0.001V and  $V_{SB}$  from 0V to 4V in steps of 1V to obtain the I-V characteristic plots.  $V_T$  values were obtained from the plot and plotted against  $V_{SB}$ .  $\gamma$  was calculated from:

$$V_T = V_{T0} + \gamma \cdot (\sqrt{\phi_s - V_{SB}} - \sqrt{\phi_s})$$

## 2.4 CMOS Inverter DC Characteristics

The netlist according to the following circuit diagram was made which included an NMOS transistor, a PMOS transistor and voltage sources.

 


Figure 2: The DC Characterization Circuit

DC analysis was performed by varying  $V_{in}$  from 0V to 3.3V in steps of 0.01V. This was done for all three:  $W_p/W_n = 60\mu m/30\mu m$ ,  $W_p/W_n = 60\mu m/60\mu m$ , and  $W_p/W_n = 30\mu m/60\mu m$ . The corresponding Switching Threshold Voltages were measured as the voltage at which  $V_{out} = V_{in}$ . Next, supply voltage,  $V_{DD}$ , was varied as 1.5 and 3V for  $W_p/W_n = 60\mu m/30\mu m$  and plots were obtained.

## 2.5 CMOS Inverter Transient Characteristics

Transient analysis was performed with a square wave input of 125MHz frequency, rise and fall times of 20ps on a CMOS Inverter having a load capacitance of 0.05pF and  $V_{DD} = 3.3V$ .

Rise and Fall times, and Propagation Delay were calculated for  $W_p/W_n = 60\mu m/30\mu m$ ,  $W_p/W_n = 60\mu m/60\mu m$ , and  $W_p/W_n = 30\mu m/60\mu m$ .

Then, The supply voltage was varied as {2, 2.2, 2.4, 2.6, 2.8, 3, 3.3}V for  $W_p/W_n = 60\mu m/30\mu m$  and propagation delays were plotted.

## 3 Simulation results

### 3.1 Code snippets

#### 3.1.1 NMOS Part 1

```
1 Vinamra Baghel 190010070 Part 1 Id-Vds Characteristics
2 .include ALD1105N.txt
3
4 *Netlist
5 M1 d g s b ALD1105N
6 Vgs g s dc 2.5
7 Vds d s dc 0
8 Vsb s b dc 0
9 Vb b 0 dc 0
10
11 *Analysis
12 .dc Vds 0 5 0.001 Vgs 2.5 4 0.5
13
14 .control
15 run
16 let Id1 = -I(Vds)[0, 5000]
17 let Id2 = -I(Vds)[5001, 10001]
18 let Id3 = -I(Vds)[10002, 15002]
19 let Id4 = -I(Vds)[15003, 20003]
20 let Vds1 = V(d)[0, 5000]
21 let Vds2 = V(d)[5001, 10001]
22 let Vds3 = V(d)[10002, 15002]
23 let Vds4 = V(d)[15003, 20003]
24 plot Id1 vs Vds1 Id2 vs Vds2 Id3 vs Vds3 Id4 vs Vds4
25
26 meas dc i11 find Id1 when Vds1 = 2m
27 meas dc i12 find Id1 when Vds1 = 5m
28 let rds1 = 3m/(i12-i11)
29 meas dc i21 find Id2 when Vds2 = 2m
30 meas dc i22 find Id2 when Vds2 = 5m
31 let rds2 = 3m/(i22-i21)
32 meas dc i31 find Id3 when Vds3 = 2m
33 meas dc i32 find Id3 when Vds3 = 5m
34 let rds3 = 3m/(i32-i31)
35 meas dc i41 find Id4 when Vds4 = 2m
36 meas dc i42 find Id4 when Vds4 = 5m
37 let rds4 = 3m/(i42-i41)
38 print rds1 rds2 rds3 rds4
39
40 meas dc i511 find Id1 when Vds1 = 4900m
41 meas dc i512 find Id1 when Vds1 = 5
42 let Vo1 = (4900m*i512-5*i511)/(i512-i511)
43 let ro1 = 100m/(i512-i511)
44 meas dc i521 find Id2 when Vds2 = 4900m
45 meas dc i522 find Id2 when Vds2 = 5
```

```

46 let Vo2 = (4900m*i522-5*i521)/(i522-i521)
47 let ro2 = 100m/(i522-i521)
48 meas dc i531 find Id3 when Vds3 = 4900m
49 meas dc i532 find Id3 when Vds3 = 5
50 let Vo3 = (4900m*i532-5*i531)/(i532-i531)
51 let ro3 = 100m/(i532-i531)
52 meas dc i541 find Id4 when Vds4 = 4900m
53 meas dc i542 find Id4 when Vds4 = 5
54 let Vo4 = (4900m*i542-5*i541)/(i542-i541)
55 let ro4 = 100m/(i542-i541)
56 print Vo1 Vo2 Vo3 Vo4
57 print ro1 ro2 ro3 ro4
58 .endc
59 .end

```

### 3.1.2 NMOS Part 2

```

1 Vinamra Baghel 190010070 Part 2 Id-Vgs Characteristics
2 .include ALD1105N.txt
3
4 *Netlist
5 M1 d g s b ALD1105N
6 Vgs g s dc 0
7 Vds d s dc 5
8 Vsb s b dc 0
9 Vb b 0 dc 0
10
11 *Analysis
12 .dc Vgs 0 5 0.001
13
14 .control
15 run
16 let Id = -I(Vds)
17 let Vdiff = V(g)-V(s)
18 plot Id vs Vdiff
19
20 meas dc Vt find Vdiff when Id = 1u
21
22 meas dc i1 find Id when Vdiff = 4
23 meas dc i2 find Id when Vdiff = 4010m
24 let gm = (i2-i1)/10m
25 print gm
26
27 let SId = sqrt(Id)
28 plot SId vs Vdiff
29 meas dc si1 find SId when Vdiff = 4
30 meas dc si2 find SId when Vdiff = 4010m
31 let k = 2*((si2-si1)/10m)^2
32 print k
33 .endc

```

```
34 .end
```

### 3.1.3 NMOS Part 3

```
1 Vinamra Baghel 190010070 Part 3 Id-Vgs Characteristics
2 .include ALD1105N.txt
3
4 *Netlist
5 M1 d g s b ALD1105N
6 Vgs g s dc 0
7 Vds d s dc 200m
8 Vsb s b dc 0
9 Vb b 0 dc 0
10
11 *Analysis
12 .dc Vgs 0 5 0.001 Vsb 0 4 1
13
14 .control
15 run
16 let Id1 = -I(Vds)[0, 5000]
17 let Id2 = -I(Vds)[5001, 10001]
18 let Id3 = -I(Vds)[10002, 15002]
19 let Id4 = -I(Vds)[15003, 20003]
20 let Id5 = -I(Vds)[20004, 25004]
21 let Vdiff = V(g)[0, 5000]-V(s)[0, 5000]
22
23 plot Id1 vs Vdiff Id2 vs Vdiff Id3 vs Vdiff Id4 vs Vdiff Id5 vs
    Vdiff
24
25 meas dc Vt1 find Vdiff when Id1 = 1u
26 meas dc Vt2 find Vdiff when Id2 = 1u
27 meas dc Vt3 find Vdiff when Id3 = 1u
28 meas dc Vt4 find Vdiff when Id4 = 1u
29 meas dc Vt5 find Vdiff when Id5 = 1u
30 print Vt1 Vt2 Vt3 Vt4 Vt5
31 .endc
32 .end
```

### 3.1.4 CMOS1

```
1 Vinamra Baghel 190010070 CMOS Inverter
2 .include CMOS.txt
3
4 *Netlist
5 M11 out1 in dd dd cmosp L=0.4u W=60u AS={2*60u*0.4u} PS={2*60u
    +4*0.4u} AD={2*60u*0.4u} PD={2*60u+4*0.4u}
6 M12 out1 in 0 0 cmosn L=0.4u W=30u AS={2*30u*0.4u} PS={2*30u+4*0.4u
    } AD={2*30u*0.4u} PD={2*30u+4*0.4u}
7 C11 out1 0 0.05p
8
```

```

9 M21 out2 in dd dd cmosp L=0.4u W=60u AS={2*60u*0.4u} PS={2*60u
  +4*0.4u} AD={2*60u*0.4u} PD={2*60u+4*0.4u}
10 M22 out2 in 0 0 cmosn L=0.4u W=60u AS={2*60u*0.4u} PS={2*60u+4*0.4u
  } AD={2*60u*0.4u} PD={2*60u+4*0.4u}
11 Cl2 out2 0 0.05p
12
13 M31 out3 in dd dd cmosp L=0.4u W=30u AS={2*30u*0.4u} PS={2*30u
  +4*0.4u} AD={2*30u*0.4u} PD={2*30u+4*0.4u}
14 M32 out3 in 0 0 cmosn L=0.4u W=60u AS={2*60u*0.4u} PS={2*60u+4*0.4u
  } AD={2*60u*0.4u} PD={2*60u+4*0.4u}
15 Cl3 out3 0 0.05p
16
17 Vdd dd 0 3.3
18 Vin in 0 0
19
20 *Analysis
21 .dc Vin 0 3.3 0.01
22
23 .control
24 run
25 plot V(out1) vs V(in) V(out2) vs V(in) V(out3) vs V(in)
26 meas dc Vth1 find V(out1) when V(out1)=V(in)
27 meas dc Vth2 find V(out2) when V(out2)=V(in)
28 meas dc Vth3 find V(out3) when V(out3)=V(in)
29 print Vth1 Vth2 Vth3
30 .endc
31 .end

```

### 3.1.5 CMOS2

```

1 Vinamra Baghel 190010070 CMOS Inverter
2 .include CMOS.txt
3
4 *Netlist
5 M11 out1 in dd dd cmosp L=0.4u W=60u AS={2*60u*0.4u} PS={2*60u
  +4*0.4u} AD={2*60u*0.4u} PD={2*60u+4*0.4u}
6 M12 out1 in 0 0 cmosn L=0.4u W=30u AS={2*30u*0.4u} PS={2*30u+4*0.4u
  } AD={2*30u*0.4u} PD={2*30u+4*0.4u}
7 Cl1 out1 0 0.05p
8
9 Vdd dd 0 3.3
10 Vin in 0 0
11
12 *Analysis
13 .dc Vin 0 3.3 0.01 Vdd 1.5 3 1.5
14
15 .control
16 run
17 let Vout1 = V(out1)[0, 330]
18 let Vout2 = V(out1)[331, 661]

```

```

19 plot Vout1 vs V(in)[0, 330] Vout2 vs V(in)[331, 661]
20 .endc
21 .end

```

### 3.1.6 CMOS3

```

1 Vinamra Baghel 190010070 CMOS Inverter Transient Characteristics
2 .include CMOS.txt
3
4 *Netlist
5 M11 out1 in dd dd cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
6 M12 out1 in 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
7 Cl1 out1 0 0.05p
8
9 M21 out2 in dd dd cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
10 M22 out2 in 0 0 cmosn L=0.4u W=60u AS=48p PS=121.6u AD=48p PD=121.6
   u
11 Cl2 out2 0 0.05p
12
13 M31 out3 in dd dd cmosp L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6
   u
14 M32 out3 in 0 0 cmosn L=0.4u W=60u AS=48p PS=121.6u AD=48p PD=121.6
   u
15 Cl3 out3 0 0.05p
16
17 Vdd dd 0 3.3
18 Vin in 0 pulse(0 3.3 0 20p 20p 4n 8n 0)
19
20 *Analysis
21 .tran 0.01n 10n
22
23 .control
24 run
25 plot V(in) V(out1) V(out2) V(out3)
26
27 meas tran tr1 trig V(out1) val=0.1*3.3 td=0 rise=1 targ V(out1) val
   =0.9*3.3 td=0 rise=1
28 meas tran tf1 trig V(out1) val=0.9*3.3 td=0 fall=2 targ V(out1) val
   =0.1*3.3 td=0 fall=2
29 meas tran tr2 trig V(out2) val=0.1*3.3 td=0 rise=1 targ V(out2) val
   =0.9*3.3 td=0 rise=1
30 meas tran tf2 trig V(out2) val=0.9*3.3 td=0 fall=2 targ V(out2) val
   =0.1*3.3 td=0 fall=2
31 meas tran tr3 trig V(out3) val=0.1*3.3 td=0 rise=1 targ V(out3) val
   =0.9*3.3 td=0 rise=1
32 meas tran tf3 trig V(out3) val=0.9*3.3 td=0 fall=2 targ V(out3) val
   =0.1*3.3 td=0 fall=2
33 print tr1 tf1 tr2 tf2 tr3 tf3

```



```

34
35 meas tran tin when V(in)=1.65
36 meas tran tout1 when V(out1)=1.65
37 print tout1-tin
38 meas tran tout2 when V(out2)=1.65
39 print tout2-tin
40 meas tran tout3 when V(out3)=1.65
41 print tout3-tin
42 .endc
43 .end

```

### 3.1.7 CMOS4

```

1 Vinamra Baghel 190010070 CMOS Inverter Transient Characteristics
2 .include CMOS.txt
3
4 *Netlist
5 M11 out1 in1 dd1 dd1 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
6 M12 out1 in1 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
7 Cl1 out1 0 0.05p
8 Vdd1 dd1 0 2
9 Vin1 in1 0 pulse(0 2 0 20p 20p 4n 8n 0)
10
11 M21 out2 in2 dd2 dd2 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
12 M22 out2 in2 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
13 Cl2 out2 0 0.05p
14 Vdd2 dd2 0 2.2
15 Vin2 in2 0 pulse(0 2.2 0 20p 20p 4n 8n 0)
16
17 M31 out3 in3 dd3 dd3 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
18 M32 out3 in3 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
19 Cl3 out3 0 0.05p
20 Vdd3 dd3 0 2.4
21 Vin3 in3 0 pulse(0 2.4 0 20p 20p 4n 8n 0)
22
23 M41 out4 in4 dd4 dd4 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
24 M42 out4 in4 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
25 Cl4 out4 0 0.05p
26 Vdd4 dd4 0 2.6
27 Vin4 in4 0 pulse(0 2.6 0 20p 20p 4n 8n 0)
28
29 M51 out5 in5 dd5 dd5 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
   =121.6u
30 M52 out5 in5 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
31 Cl5 out5 0 0.05p
32 Vdd5 dd5 0 2.8

```

```

33 Vin5 in5 0 pulse(0 2.8 0 20p 20p 4n 8n 0)
34
35 M61 out6 in6 dd6 dd6 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
    =121.6u
36 M62 out6 in6 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
37 Cl6 out6 0 0.05p
38 Vdd6 dd6 0 3
39 Vin6 in6 0 pulse(0 3 0 20p 20p 4n 8n 0)
40
41 M71 out7 in7 dd7 dd7 cmosp L=0.4u W=60u AS=48p PS=121.6u AD=48p PD
    =121.6u
42 M72 out7 in7 0 0 cmosn L=0.4u W=30u AS=24p PS=61.6u AD=24p PD=61.6u
43 Cl7 out7 0 0.05p
44 Vdd7 dd7 0 3.3
45 Vin7 in7 0 pulse(0 3.3 0 20p 20p 4n 8n 0)
46
47 *Analysis
48 .tran 0.1n 20n
49
50 .control
51 run
52 meas tran tin1 when V(in1)=1
53 meas tran tin2 when V(in2)=1.1
54 meas tran tin3 when V(in3)=1.2
55 meas tran tin4 when V(in4)=1.3
56 meas tran tin5 when V(in5)=1.4
57 meas tran tin6 when V(in6)=1.5
58 meas tran tin7 when V(in7)=1.65
59 meas tran tout1 when V(out1)=1
60 meas tran tout2 when V(out2)=1.1
61 meas tran tout3 when V(out3)=1.2
62 meas tran tout4 when V(out4)=1.3
63 meas tran tout5 when V(out5)=1.4
64 meas tran tout6 when V(out6)=1.5
65 meas tran tout7 when V(out7)=1.65
66 let tp1 = tout1-tin1
67 let tp2 = tout2-tin2
68 let tp3 = tout3-tin3
69 let tp4 = tout4-tin4
70 let tp5 = tout5-tin5
71 let tp6 = tout6-tin6
72 let tp7 = tout7-tin7
73 print tp1 tp2 tp3 tp4 tp5 tp6 tp7
74 .endc
75 .end

```

## 3.2 Simulation results

### 3.2.1 Part 1



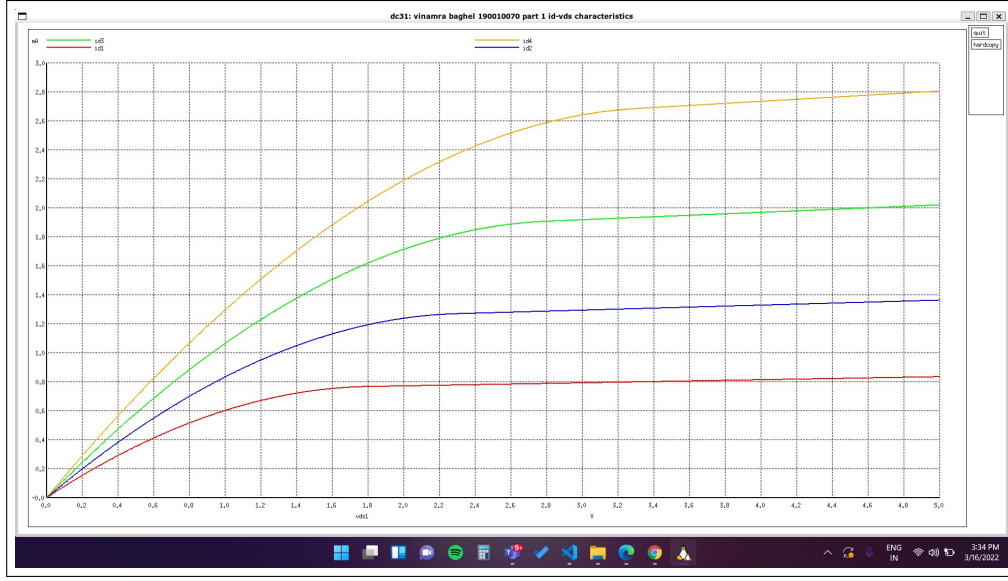


Figure 3:  $I_D - V_{DS}$  Characteristics

### 3.2.2 Part 2

 


(a)  $I_D - V_{GS}$

 


(b)  $\sqrt{I_D} - V_{GS}$

Figure 4:  $I_D - V_{GS}$  and  $\sqrt{I_D} - V_{GS}$  Characteristics for  $V_{DS} = 200mV$

 

(a)  $I_D - V_{GS}$

 

(b)  $\sqrt{I_D} - V_{GS}$

Figure 5:  $I_D - V_{GS}$  and  $\sqrt{I_D} - V_{GS}$  Characteristics for  $V_{DS} = 5V$

3.2.3 Part 3

 


Figure 6:  $I_D - V_{GS}$  Characteristics for different  $V_{SB}$

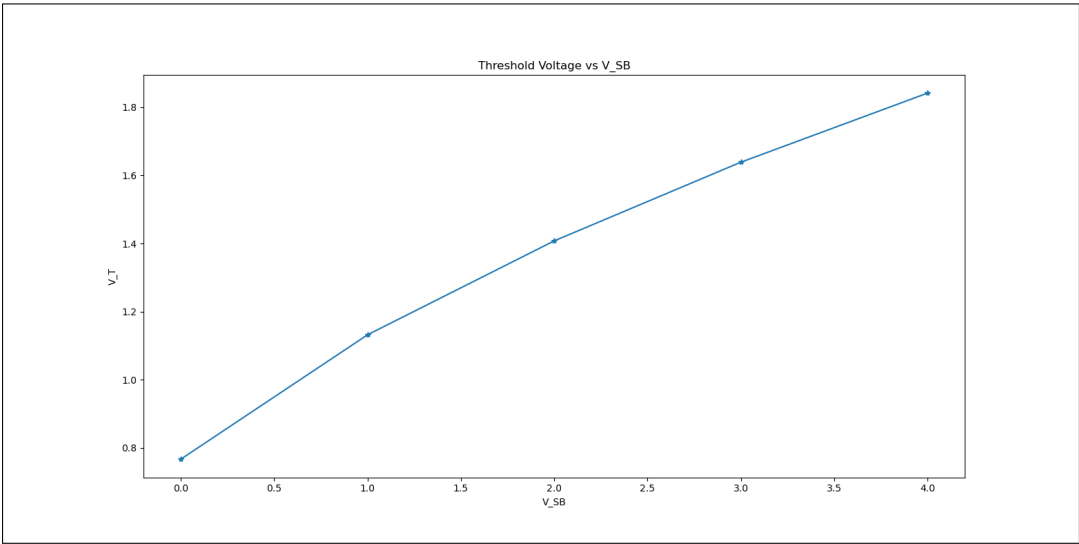


Figure 7: Threshold Voltage vs  $V_{SB}$

### 3.2.4 CMOS Inverter DC Characteristics

 


Figure 8: DC Characteristics of CMOS Inverter for different  $W_p/W_n$  values

The Switching Threshold Voltage decreases with decreasing  $W_p/W_n$ . **Index:**

- **Red:**  $W_p/W_n = 60\mu m/30\mu m$
- **Blue:**  $W_p/W_n = 60\mu m/60\mu m$
- **Green:**  $W_p/W_n = 30\mu m/60\mu m$

 


Figure 9: DC Characteristics of CMOS Inverter for different supply voltages

The output starts at the supply voltage for LOW input and ends at 0 for HIGH. **Index:**

- **Red:** Supply voltage,  $V_{DD} = 1.5V$
- **Blue:** Supply voltage,  $V_{DD} = 3V$

### 3.2.5 CMOS Inverter Transient Characteristics

 


Figure 10: CMOS Inverter Switching Transient Characteristics

Index:

- Red:  $V_{in}$
- Blue:  $V_{out}$  for  $W_p/W_n = 60\mu m/60\mu m$
- Green:  $V_{out}$  for  $W_p/W_n = 30\mu m/60\mu m$
- Orange:  $V_{out}$  for  $W_p/W_n = 30\mu m/60\mu m$

Talking about the Rise Time, Fall Time, and Propagation Delay for decreasing  $W_p/W_n$ : Rise time **increases**, Fall time **decreases**, and Propagation delay **decreases**.

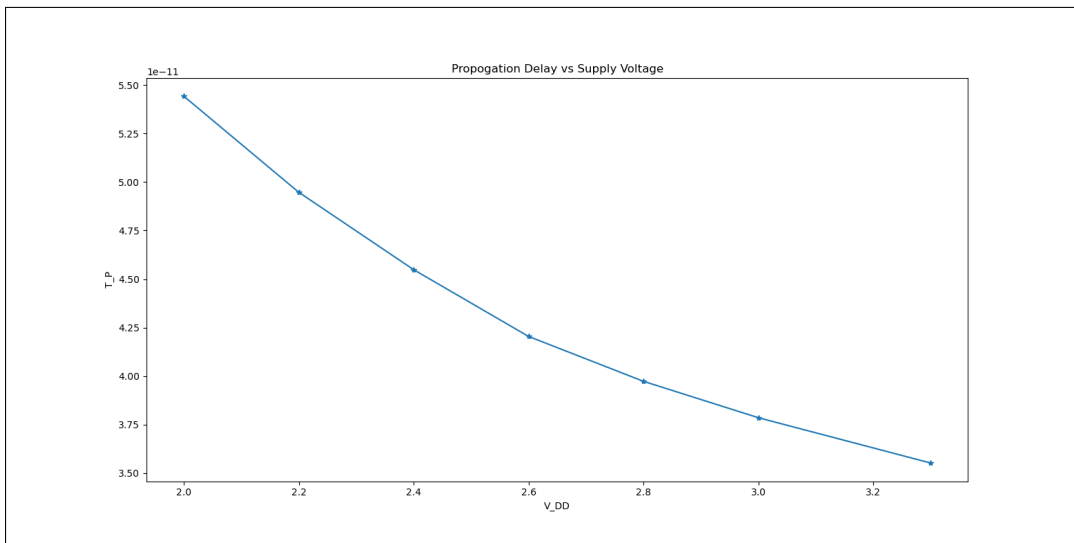


Figure 11: Propagation Delay vs Supply Voltage

The propagation delay **decreases** with an increase in supply voltage.

## 4 Experimental results

**Part 1:**  $R_{DS}$ ,  $V_0$  and  $r_0$ .

$V_{GS}$ (in V)	$R_{DS}$ (in $k\Omega$ )	$V_0$ (in V)	$r_0$ (in $k\Omega$ )
<b>2.5</b>	1.237	-34.483	47.301
<b>3</b>	0.967	-34.491	28.977
<b>3.5</b>	0.794	-34.480	19.547
<b>4</b>	0.674	-34.487	14.075

**Part 2:**  $V_T$ ,  $g_m$  and  $k$ .

For  $V_{DS} = 200mV$ ,

$V_T = 0.766V$ ,  $g_m = 9.052 \times 10^{-5}\Omega^{-1}$  and  $k = 1.412 \times 10^{-5}AV^{-2}$ .

For  $V_{DS} = 5V$ ,

$V_T = 0.762V$ ,  $g_m = 1.703 \times 10^{-3}\Omega^{-1}$  and  $k = 5.153 \times 10^{-4}AV^{-2}$ .

**Part 3:** The  $V_{Ts}$  for  $V_{SB} = \{0, 1, 2, 3, 4\}$  respectively are:

**0.766, 1.132, 1.408, 1.639, and 1.842.**

The value of  $\gamma$  came out to be **0.785**.

**CMOS DC Characteristics:**

Switching Threshold Voltages for  $W_p/W_n = 60\mu m/30\mu m$ ,  $W_p/W_n = 60\mu m/60\mu m$ , and  $W_p/W_n = 30\mu m/60\mu m$  respectively: **1.609V, 1.393V, 1.204V**.

**CMOS Transient Characteristics:**

$W_p/W_n$	Rise Time (in $ps$ )	Fall Time (in $ps$ )	Propagation Delay (in $ps$ )
$60\mu m/30\mu m$	8.499	27.776	35.287
$60\mu m/60\mu m$	10.940	18.394	23.954
$30\mu m/60\mu m$	18.514	15.540	19.382

Supply Voltage (in V)	Propagation Delay (in $ps$ )
2	54.423
2.2	49.475
2.4	45.486
2.6	42.047
2.8	39.734
3	37.859
3.3	35.523

## 5 Experiment completion status

I could complete all the parts of the lab. There was no hardware involvement as it was all simulation based. The results were shown to the TA and then submitted.