

# EE 236: Experiment No. 0

## NgSpice Introduction

Vinamra Baghel, 190010070

January 9, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

The experiment aimed at providing the students with an introduction to the circuit simulation software **NgSpice** through hands-on implementation and simulation of certain circuits. The experiment entailed the students to go through the given solved examples in a shared PPT and solve 2 given exercises:

1. Switching polarities of the (a) diode and (b) 2V battery in a shunt clipper and observing the output voltage waveform and the  $V_{out}$  vs  $V_{in}$  characteristics for a 1 kHz sinusoidal input voltage.
2. Designing a diode-based Bridge Rectifier and simulating it for a 12V 50Hz input voltage, hence obtaining the  $V_{out}$  vs  $V_{in}$  characteristics.

### 1.2 Methods

The method for both the parts included making the circuit diagram, writing the netlist for the circuit in a CIR file, writing the analysis command (`.tran`) and running it to obtain the plots asked for in the exercise. The first part involved constructing a shunt clipper, whose diagram was given in the handout. The netlist was based on that. The second part required us to construct a bridge rectifier on our own.

## 2 Design

### 2.1 Shunt Clipper

The NgSpice code was based on the diagram given in the handout, provided below. The netlist included the 1N914 diode, a 2V battery, a 1 k $\Omega$  resistor and input voltage (10V in this case). To obtain the  $V_{out}$  vs  $V_{in}$  characteristics, one could have done DC analysis but I chose to go for Transient analysis to obtain the output waveform  $V_{out}$  as well. The shunt clipper produces an output voltage which is a clipped version of the input voltage (clipped at 2+0.7 volts).



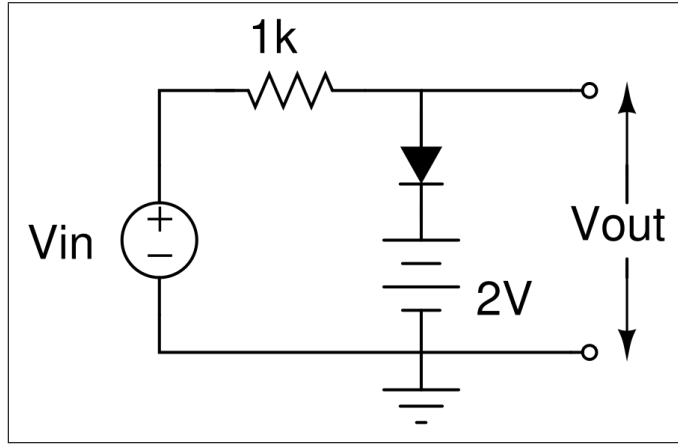


Figure 1: Shunt Clipper

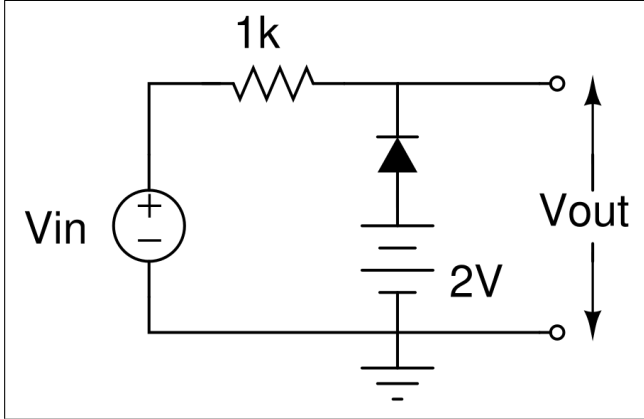In the first part, we reverse the diode polarity. The circuit clips at  $2 - 0.7$  volts. In the second part, we reverse the battery polarity. The circuit clips at  $-2 - 0.7$  volts.



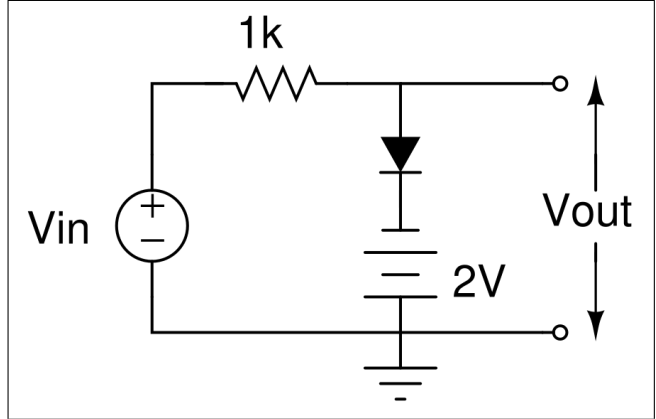(a) Shunt Clipper with diode polarity reversed



(b) Shunt Clipper with battery polarity reversed

## 2.2 Bridge Rectifier

A bridge rectifier is used to obtain positive waves by converting the negative parts of the input wave to positive. The netlist included a resistor, input voltage (12V, 50Hz) and 4 diodes. Transient analysis was performed to obtain the  $V_{out}$  and  $V_{out}$  vs  $V_{in}$  waveforms.

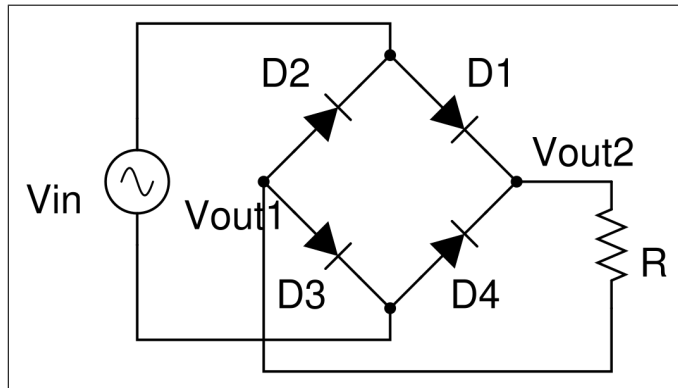


Figure 3: Bridge Rectifier

## 3 Simulation results

### 3.1 Code snippet

#### 3.1.1 Shunt Clipper

```
Vinamra Baghel 190010070 Shunt Clipper
.include Diode_1N914.txt
Netlist
r1 in out 1k
D b out 1N914
Vb b gnd 2
Vin in gnd sin(0 10 1k 0 0 0)
Analysis
.tran 1u 6m
Control
.control
run
plot V(out) vs V(in)
.endc
.end
```


#### 3.1.2 Bridge Rectifier

```
Vinamra Baghel 190010070 Bridge Rectifier
.include Diode_1N914.txt
Netlist
rl out1 out2 1k
D1 in out2 1N914
D2 out1 in 1N914
D3 out1 gnd 1N914
D4 gnd out2 1N914
Vin in gnd sin(0 12 50 0 0 0)
Analysis
.tran 1u 60m
Control
.control
run
plot V(out2) - V(out1) vs V(in)
.endc
.end
```


### 3.2 Simulation results
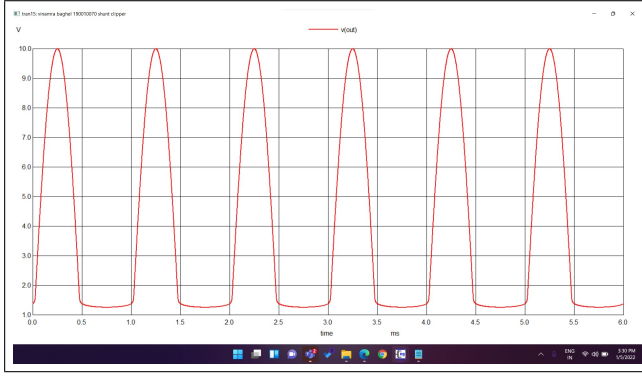
#### 3.2.1 Shunt Clipper

The first part required us to reverse the diode polarity while the second part required us to reverse the battery polarity. The plots obtained are as follow.




(a)  $V_{out}$  vs  $t$

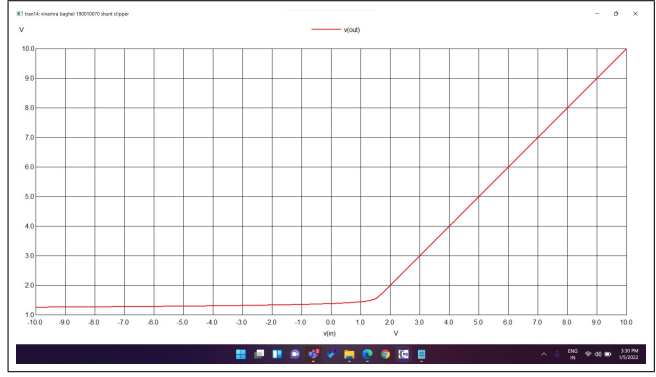


(b)  $V_{out}$  vs  $V_{in}$

Figure 4: Shunt Clipper with diode polarity reversed

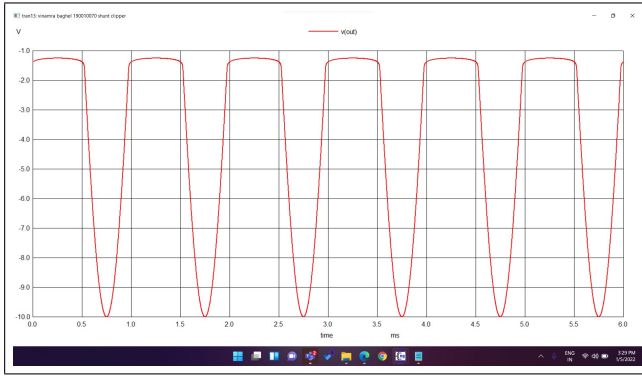

(a)  $V_{out}$  vs  $t$

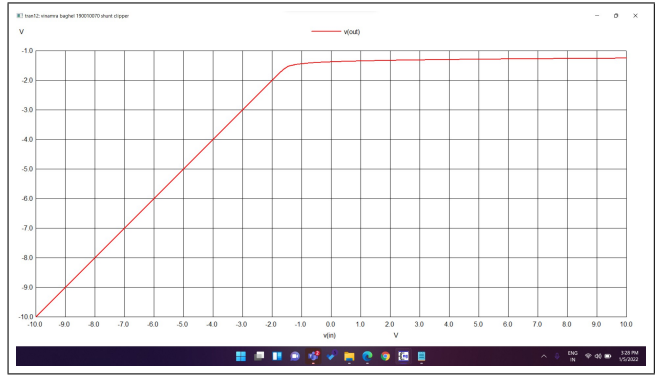


(b)  $V_{out}$  vs  $V_{in}$


Figure 5: Shunt Clipper with battery polarity reversed
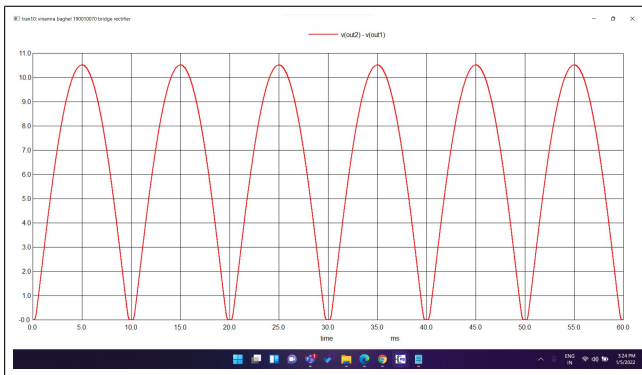
### 3.2.2 Bridge Rectifier

We were required to plot and simulate a diode-based bridge rectifier. The plots are as follow.



(a)  $V_{out}$  vs  $t$

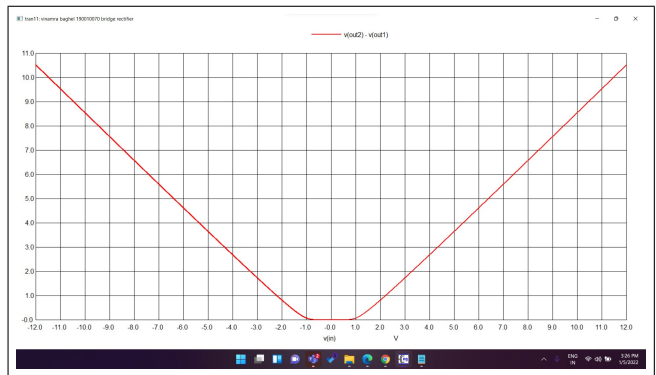

(b)  $V_{out}$  vs  $V_{in}$

Figure 6: Bridge Rectifier

## 4 Experiment completion status

I could complete both the exercises given in the lab. There was no hardware involvement as it was all simulation based. The results were shown to the TA and then submitted.