

EE 236: Experiment No. 5

PMOS I-V Characteristics and Applications

Vinamra Baghel, 190010070

March 9, 2022

1 Overview of the experiment

1.1 Aim of the experiment

The following were the aims of the experiment:

- To measure transfer characteristics of PMOS transistor.
- To analyse the effect of body bias on the characteristics of a PMOS transistor.

1.2 Methods

The method overview includes constructing circuit netlists according to the standard circuit, simulating them using *dc* analysis and calculating required parameters for all parts. The first plot required us to plot $I_D - V_{DS}$ characteristics, and calculate r_{DS} , Early Voltage (V_0), and r_0 . The second and third plots required us to plot $I_D - V_{GS}$ characteristics, and find V_T , g_m and k .

2 Design

2.1 Part 1

The netlist according to the following circuit diagram was made which included a PMOS transistor and voltage sources.

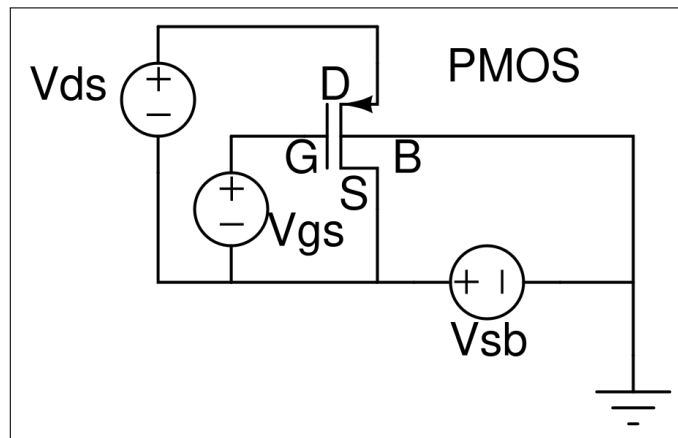


Figure 1: The I-V Characterization Circuit

DC analysis was performed by varying V_{DS} from 0V to -5V in steps of -0.001V and V_{GS} from -2.5V to -4V in steps of -0.5V to obtain the I-V characteristic plots. R_{DS} in the linear region was found using:

$$R_{DS} = \frac{\Delta V_{DS}}{\Delta I_{DS}}$$

V_0 was found as the x-intercept of the equation in the saturation region:

$$y = mx + c$$

R_0 in the saturation region was found using:

$$R_0 = \frac{\Delta V_{DS}}{\Delta I_{DS}}$$

2.2 Part 2

I_D was plotted against V_{GS} , first keeping $V_{DS} = -200mV$ (linear) and then $V_{DS} = -5V$ (saturation). V_T and g_m were found from the plot.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Then, k was found from the slope of the $\sqrt{I_D}$ vs V_{GS} .

$$k = 2. \left(\frac{\Delta \sqrt{I_D}}{\Delta V_{GS}} \right)^2$$

2.3 Part 3

V_{DS} was set to -200mV. DC analysis was performed by varying V_{GS} from 0V to -5V in steps of -0.01V and V_{SB} from 0V to -4V in steps of -V to obtain the I-V characteristic plots. V_T values were obtained from the plot and plotted against V_{SB} . γ was calculated from:

$$V_T = V_{T0} + \gamma.(\sqrt{\phi_s - V_{SB}} - \sqrt{\phi_s})$$

3 Simulation results

3.1 Code snippets

3.1.1 Part 1

```
1 Vinamra Baghel 190010070 Part 1 Id-Vds Characteristics
2 .include pmos.txt
3
4 *Netlist
5 M1 d g 0 0 ALD1107
6 Vg g 0 dc -2.5
7 Vd d 0 dc 0
8
9 *Analysis
10 .dc Vd 0 -5 -1m Vg -2.5 -4 -0.5
11
12 .control
13 run
14 let Id1 = I(Vd)[0, 5000]
15 let Id2 = I(Vd)[5001, 10001]
16 let Id3 = I(Vd)[10002, 15002]
17 let Id4 = I(Vd)[15003, 20003]
18 let Vds1 = V(d)[0, 5000]
19 let Vds2 = V(d)[5001, 10001]
20 let Vds3 = V(d)[10002, 15002]
21 let Vds4 = V(d)[15003, 20003]
22 plot Id1 vs Vds1 Id2 vs Vds2 Id3 vs Vds3 Id4 vs Vds4
23
24 meas dc i11 find Id1 when Vds1 = -1m
25 meas dc i12 find Id1 when Vds1 = -2m
26 let rds1 = 1m/(i12-i11)
27 meas dc i21 find Id2 when Vds2 = -1m
28 meas dc i22 find Id2 when Vds2 = -2m
29 let rds2 = 1m/(i22-i21)
30 meas dc i31 find Id3 when Vds3 = -1m
31 meas dc i32 find Id3 when Vds3 = -2m
32 let rds3 = 1m/(i32-i31)
33 meas dc i41 find Id4 when Vds4 = -1m
34 meas dc i42 find Id4 when Vds4 = -2m
35 let rds4 = 1m/(i42-i41)
36
37 print rds1 rds2 rds3 rds4
38
39 meas dc i511 find Id1 when Vds1 = -4900m
40 meas dc i512 find Id1 when Vds1 = -5
41 let Vo1 = (-4900m*i512-(-5)*i511)/(i512-i511)
42 let ro1 = 100m/(i512-i511)
43 meas dc i521 find Id2 when Vds2 = -4900m
44 meas dc i522 find Id2 when Vds2 = -5
45 let Vo2 = (-4900m*i522-(-5)*i521)/(i522-i521)
```

```

46 let ro2 = 100m/(i522-i521)
47 meas dc i531 find Id3 when Vds3 = -4900m
48 meas dc i532 find Id3 when Vds3 = -5
49 let Vo3 = (-4900m*i532-(-5)*i531)/(i532-i531)
50 let ro3 = 100m/(i532-i531)
51 meas dc i541 find Id4 when Vds4 = -4900m
52 meas dc i542 find Id4 when Vds4 = -5
53 let Vo4 = (-4900m*i542-(-5)*i541)/(i542-i541)
54 let ro4 = 100m/(i542-i541)
55
56 print Vo1 Vo2 Vo3 Vo4
57 print ro1 ro2 ro3 ro4
58 .endc
59 .end

```

3.1.2 Part 2

```

1 Vinamra Baghel 190010070 Part 2 Id-Vgs Characteristics
2 .include pmos.txt
3
4 *Netlist
5 M1 d g 0 0 ALD1107
6 Vg g 0 dc -5
7 Vd d 0 dc -200m
8
9 *Analysis
10 .dc Vg -5 0 0.01
11
12 .control
13 run
14 let Id = I(Vd)
15 let Vg = V(g)
16 plot I(Vd) vs V(g)
17
18 meas dc i1 find Id when Vg = -4
19 meas dc i2 find Id when Vg = -4010m
20 let gm = (i2-i1)/10m
21 print gm
22
23 let SId = sqrt(Id)
24 plot SId vs Vg
25 meas dc si1 find SId when Vg = -4
26 meas dc si2 find SId when Vg = -4010m
27 let k = 2*((si2-si1)/10m)^2
28 print k
29 .endc
30 .end

```

3.1.3 Part 3

```

1 Vinamra Baghel 190010070 Part 3 Id-Vgs Characteristics
2 .include pmos.txt
3
4 *Netlist
5 M1 d g s b ALD1107
6 Vgs g s dc -5
7 Vds d s dc -200m
8 Vsb s b dc 0
9 Vb b 0 dc 0
10
11 *Analysis
12 .dc Vgs -5 0 0.01 Vsb 0 -4 -1
13
14 .control
15 run
16 let Id1 = I(Vds)[0, 500]
17 let Id2 = I(Vds)[501, 1001]
18 let Id3 = I(Vds)[1002, 1502]
19 let Id4 = I(Vds)[1503, 2003]
20 let Id5 = I(Vds)[2004, 2504]
21
22 plot Id1 Id2 Id3 Id4 Id5
23 .endc
24 .end

```

3.2 Simulation results

3.2.1 Part 1


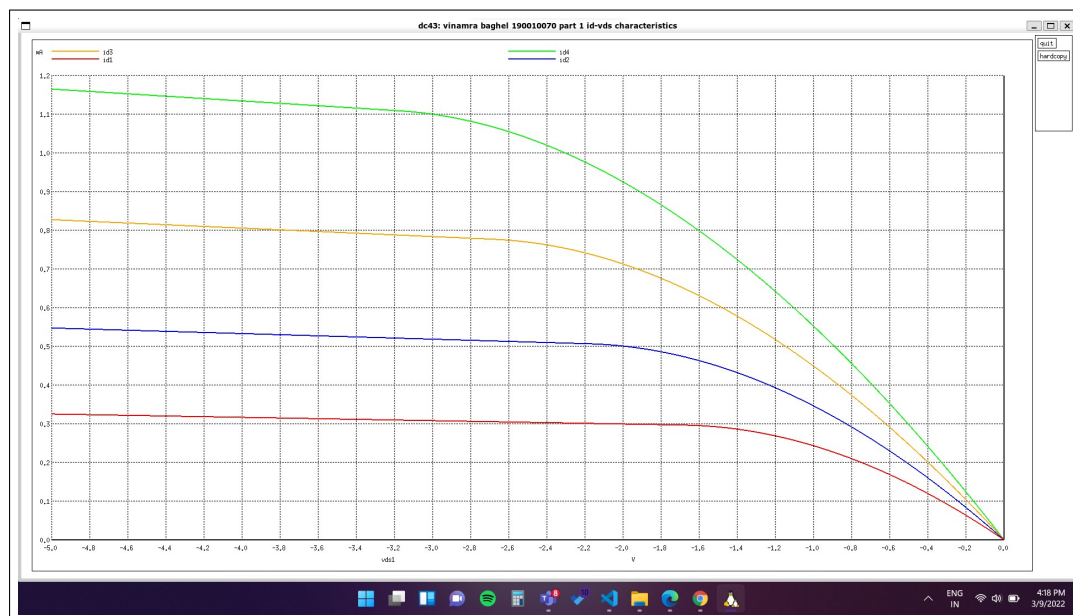



Figure 2: $I_D - V_{DS}$ Characteristics

Shown above were the $I_D - V_{DS}$ characteristics.

3.2.2 Part 2

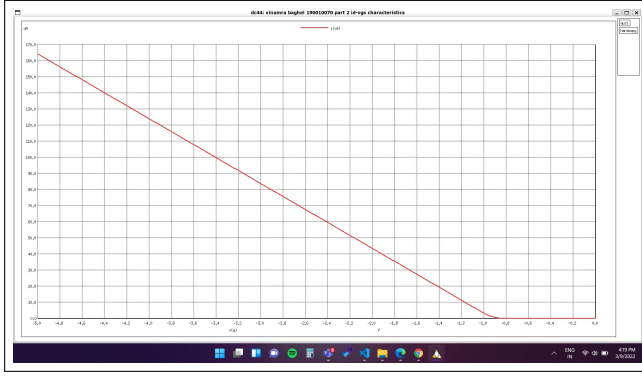


(a) $I_D - V_{GS}$

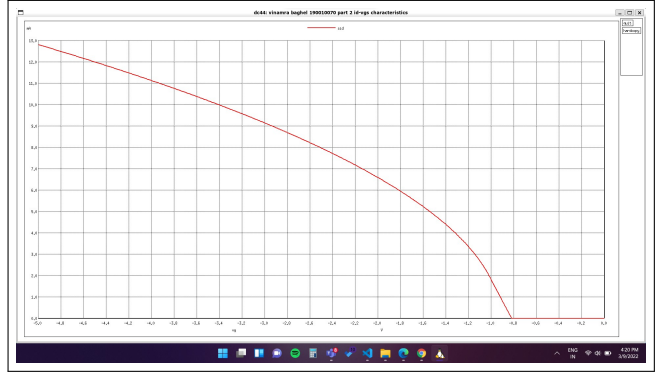


(b) $\sqrt{I_D} - V_{GS}$

Figure 3: $I_D - V_{GS}$ and $\sqrt{I_D} - V_{GS}$ Characteristics for $V_{DS} = -200mV$

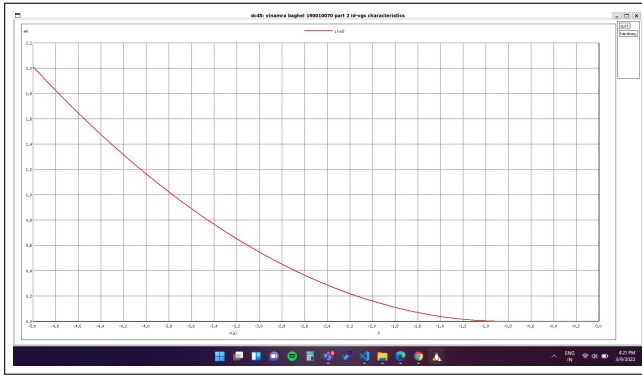

(a) $I_D - V_{GS}$

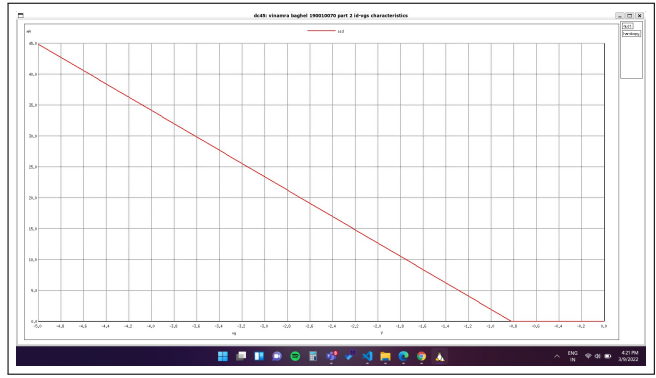

(b) $\sqrt{I_D} - V_{GS}$

Figure 4: $I_D - V_{GS}$ and $\sqrt{I_D} - V_{GS}$ Characteristics for $V_{DS} = -5V$

3.2.3 Part 3

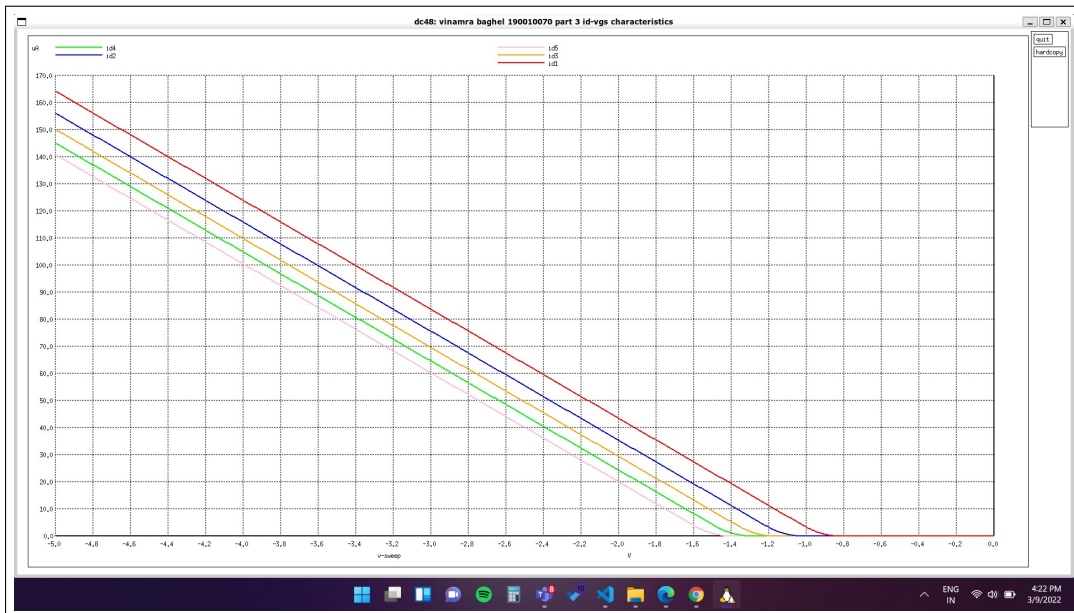


Figure 5: $I_D - V_{GS}$ Characteristics for different V_{SB}

4 Experimental results

Part 1: R_{DS} , V_0 and r_0 .

V_{GS} (in V)	R_{DS} (in $k\Omega$)	V_0 (in V)	r_0 (in $k\Omega$)
-2.5	2.979	32.895	116.550
-3	2.295	32.896	69.219
-3.5	1.867	32.894	45.798
-4	1.573	32.897	32.531

Part 2: V_T , g_m and k .

For $V_{DS} = -200mV$,

$V_T = -0.879V$, $g_m = 4.024 \times 10^{-5}\Omega^{-1}$ and $k = 6.523 \times 10^{-6}AV^{-2}$.

For $V_{DS} = -5V$,

$V_T = -1.009V$, $g_m = 7.339 \times 10^{-4}\Omega^{-1}$ and $k = 2.304 \times 10^{-4}AV^{-2}$.

Part 3: The V_{TS} for $V_{SB} = \{0, -1, -2, -3, -4\}$ respectively are:

-0.86177, -1.05588, -1.20588, -1.33235, and -1.44118.

The value of *gamma* came out to be **-0.447**.

5 Experiment completion status

I could complete all the parts of the lab. There was no hardware involvement as it was all simulation based. The results were shown to the TA and then submitted.